

LE4.2

🔖 Bookmark this page

LE4.2.1: AND of many inputs

3/3 points (ungraded)
Suppose we wanted to build a circuit to compute the AND of 1024 separate inputs. There's good news and bad news. The bad news is that we only have 2-input AND gates (called AND2) to use when implementing the circuit. The good news is that we have as many AND2 devices as we need.

The AND2 device has a contamination delay t_{CD} of 1 ns and a propagation delay t_{PD} of 4 ns.

What is the minimum number of AND2 devices needed to implement the circuit?

Minimum number of AND2 devices needed: ✓

Considering all possible implementations, what is the smallest achievable t_{CD} ?

Smallest achievable t_{CD} (in ns): ✓

Considering all possible implementations, what is the smallest achievable t_{PD} ?

Smallest achievable t_{PD} (in ns): ✓



Submit

Discussion

Hide Discussion

Topic: 4. Combinational Logic / LE4.2

Add a Post

Show all posts ▾	by recent activity ▾
 Contamination Delay?	6
How is contamination delay calculated? I must have missed this during the videos.	
 Contamination Delay Calculation regarding shortest path ?	6
Hello , In the lecture when considering the development in circuits with the help of boolean expressions we are thinking of logical bin...	

< Previous

Next >

 Calculator



edX

- [About](#)
- [Affiliates](#)
- [edX for Business](#)
- [Open edX](#)
- [Careers](#)
- [News](#)

Legal

- [Terms of Service & Honor Code](#)
- [Privacy Policy](#)
- [Accessibility Policy](#)
- [Trademark Policy](#)
- [Sitemap](#)

Connect

- [Blog](#)
- [Contact Us](#)
- [Help Center](#)
- [Media Kit](#)
- [Donate](#)



© 2021 edX Inc. All rights reserved.
深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)