

[Course](#)

[Progress](#)

[Dates](#)

[Course Notes](#)

[Discussion](#)

[🏠 Course](#) / [7. Performance Measures](#) / [Lecture Videos \(33:12\)](#)



< Previous

 ✓

 ✓



 ✓

 ✓

 ✓

 ✓

 ✓

 ✓

Next >

# LE7.3


 Bookmark this page

LE7.3.1 Pipelined Components

6/6 points (ungraded)


The Government’s energy policy revolves around the efficient repetitive execution of a simple algorithm: for various values of A and B, it must compute the quantity  $\text{Keystone}(A,B) = (A+B)*(A-B)$ . A consortium of entrepreneurs has proposed that a pipelined execution of this computation could solve the country’s problems. You have been brought in as a consultant to evaluate their proposal. The Keystone proposal, as it is called, is that a set of pipelined modules be designed to perform basic operations, and these modules be assembled to perform the required computation of  $(A+B)*(A-B)$ . It has been determined that the computation will use 32-bit two’s-complement binary numbers as the representation of A, B, and the result of the computation.

 - 1. **ADD**: a 2-stage pipeline that adds two 32-bit quantities.
- 2. **NEG**: a 1-stage pipeline that negates a single 32-bit quantity.
- 3. **MUL**: a 5-stage pipeline that multiplies two 32-bit quantities, producing a 32-bit product.
- 4. **BUF**: a 1-stage pipeline that reproduces its 32-bit input one clock cycle later.



Each of the modules is a well-formed k-pipeline for its specified k, with k registers on each input/output path (including registers on each output). For example, Keystone proponents argue that the 2-stage ADD module can be made using two 16-bit adders by adding some additional registers:

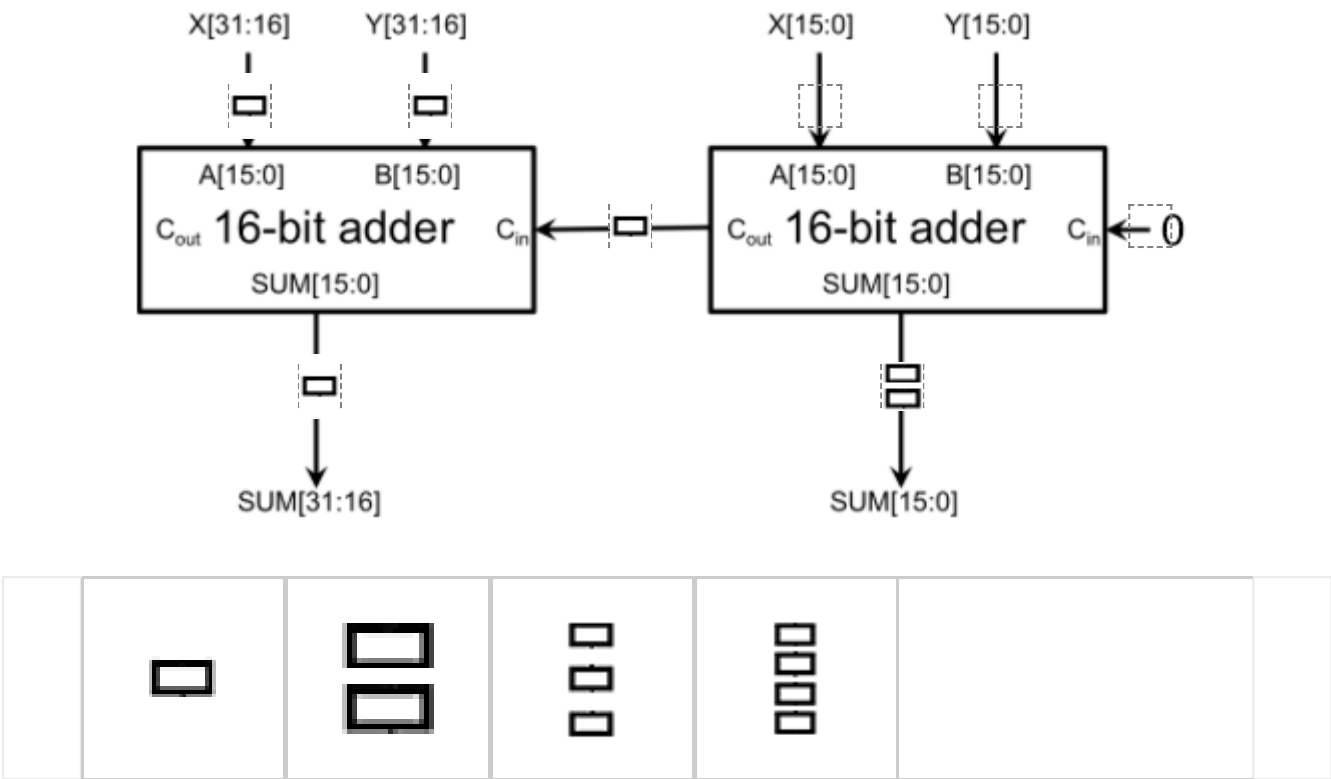Mark the locations of the minimal number of registers in the circuit below to make it a valid 2- stage pipelined ADD module while maximizing throughput. Provide your answer by dragging the correct number of pipeline registers onto each of the dashed square boxes. Be sure that each output has a register.



During a vigorous Senate investigation, an engineer was forced to admit that the BUF module performed no actual computation, but contained a 32-bit register that served only to delay its input by one clock cycle. Senator Quagmire has demanded an explanation for why taxpayers should be asked to pay for development of such a do-nothing module.


- ☐ The extra registers are required to restore marginally-valid digital signals.
- ☐ Additional registers are inserted to satisfy hold time requirements.
- ☒ Well-formed pipelines may require “do-nothing” pipeline stages.
- ☐ You’re absolutely right, Sir. We’ll eliminate the BUF module immediately.



Keystone proponents propose a specific implementation for the pipelined computation, using their module toolkit:

In a candid interview on Cheat the Press, one of the Keystone group admits that he is not 100% sure that provided schematic will work. His exact quote: “We tried to hire a 6.004x student, but they were all studying for some dumb exam!”. Your chance to be a hero.

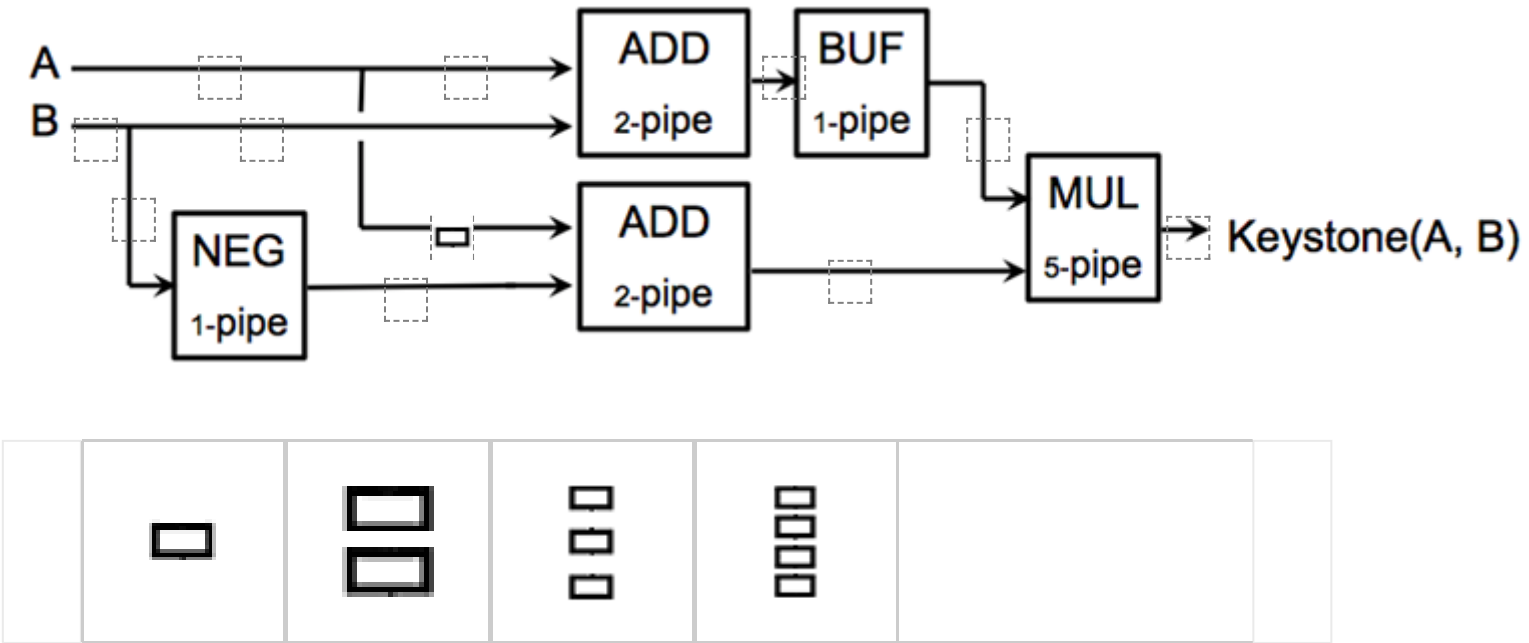Is the diagram below a well-formed pipeline? If yes, do not add any wasteful buffers, and submit the diagram as-is. If not, show where to add a minimal number of BUF modules to make it well formed. For this problem treat each drag and drop register as a BUF module.



Assume that the clock period is 1 ns. What is the latency of the pipeline (with your fixes, if any)? What is the throughput?

Latency (ns):  ✓

Throughput (1/ns):  ✓

The pipeline (with any amendments you suggested) is built at great cost, and works. But, at the last minute, it is learned that a the computation really needed is Keystone(XL(A), B) rather than Keystone(A,B): an extra XL stage must be added to the pipeline. The Government finds a combinational XL module whose  $t_{pd}$  is nearly 3 ns, but the XL module can't be pipelined. They insist that they need to maintain the pipeline's throughput, and again ask your advice on how to keep the current throughput while minimizing cost. How would you advise them to proceed?

- ☐ Make a 1-stage pipelined XL by adding registers, and run with a 3ns clock period.
- ☐ Construct a total of three Keystone(XL(A), B) pipelines, each with a 3ns clock period.
- ☐ Remove all registers, and use a strictly combinational implementation.
- ☒ Use 3 combinational XL modules and some logic to emulate a 3-stage pipelined XL module, and add that to the existing pipeline.
- ☐ Tell them that it's impossible to meet the updated specifications, and that they should have specified all of the circuit requirements before calling you in to provide a solution.



Submit

Discussion

Hide Discussion

Topic: 7. Performance Measures / LE7.3

Add a Post

<div><div>?</div><div>About First Question</div></div>	<div>I don't understand anything about why we add "two register" to output of low-order 16 bits (right side) in order to produce a 32-bit a...</div>	<div>2</div> <div></div>
<div><div>✓</div><div>Register at the output of Keystone</div></div>	<div>Why there is no register at the output of the Keystone circuit? I thought that the agreement is to have a register at the end of each o...</div>	<div>3</div> <div></div>



## edX

- About
- Affiliates
- edX for Business
- Open edX
- Careers
- News

## Legal

- Terms of Service & Honor Code
- Privacy Policy
- Accessibility Policy
- Trademark Policy
- Sitemap

## Connect

- Blog
- Contact Us
- Help Center
- Media Kit
- Donate

