







< Previous	 ✓	 ✓	 ✓	 ✓	Next >
------------	---	---	---	---	--------


### WE4.3

 Bookmark this page

Video explanation of solution is provided below the problem.

Combinational Logic Timing

2/2 points (ungraded)

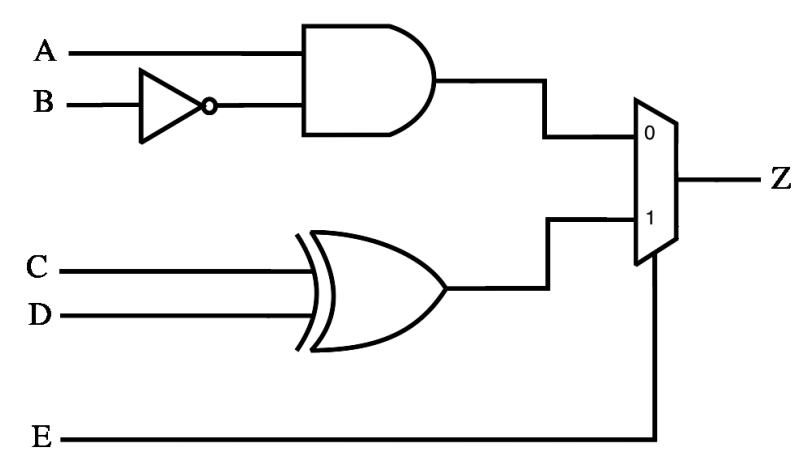

Here's a table showing the  $t_{CD}$  and  $t_{PD}$  for each of the components in the circuit above. Please compute  $t_{CD}$  and  $t_{PD}$  for the circuit as a whole.

	$t_{CD}$	$t_{PD}$
Inverter	0.2 ns	0.6 ns
AND2	0.3 ns	1.0 ns
XOR2	0.7 ns	1.7 ns
MUX2	0.4 ns	1.4 ns

$t_{CD}$  (ns):

✓

$t_{PD}$  (ns):

✓

Submit

Combinational Logic Timing

# Combinational Logic Timing

(Caption will be displayed when you start playing the video.)

Calculator

AND2	0.2 ns	1.2 ns
XOR2	0.4 ns	2.1 ns
MUX2	0.2 ns	1.5 ns

0:00 / 0:00

1.0x

Video

[Download video file](#)

Transcripts

[Download SubRip \(.srt\) file](#)

[Download Text \(.txt\) file](#)

Discussion

Hide Discussion

Topic: 4. Combinational Logic / WE4.3

Add a Post

Show all posts

by recent activity

[Seems to be needed some adjustment](#)

2

['Submit' button not working.](#)  
[The 'Submit' option isn't working for me. Neither it's showing the correct answer.](#)

4

< Previous

Next >



edX

- [About](#)
- [Affiliates](#)
- [edX for Business](#)
- [Open edX](#)
- [Careers](#)
- [News](#)

Legal

- [Terms of Service & Honor Code](#)
- [Privacy Policy](#)
- [Accessibility Policy](#)
- [Trademark Policy](#)
- [Sitemap](#)

Connect

Calculator

[Blog](#)

[Contact Us](#)

[Help Center](#)

[Media Kit](#)

[Donate](#)



© 2021 edX Inc. All rights reserved.  
深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)