



< Previous	 ✓	 ✓	 ✓	Next >
------------	---	---	---	--------

### Tutorial : Minimal Sum Of Products


 Bookmark this page

For the following problems, please use the following conventions when entering boolean expressions.

- $\bar{X}$ : enter as not(X).
- X AND Y: enter as XY.
- X AND  $\bar{Y}$ : enter as Xnot(Y).
- X OR Y: enter as X + Y.
- $\bar{X}\bar{Y}$ : enter as not(X)not(Y).
- Recall that  $\overline{XY} = \bar{X} + \bar{Y}$  (not  $\bar{X}\bar{Y}$ ).
- Extra white spaces are ignored.
- Lower or upper case letters are treated the same.
- Sum of products expression refers to an expression of the form  $ABC + \text{not}(A)\text{not}(B)C$ , where each term is a product term and ORing them together makes a sum of products expression. Note that within a product term negation can only be applied to a single variable at a time. In other words not(A)not(B) is acceptable but not(AB) is not.

Minimal Sum Of Products

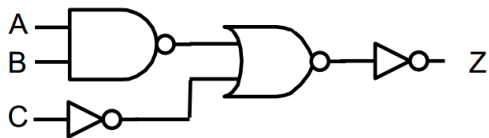1/1 point (ungraded)  
Consider the following circuit that implements the 3-input function Z(A,B,C):



What is the minimal sum-of-products expression for Z(A,B,C):

not(a) + not(b) + not(c) ✓

Submit

Minimal Sum Of Products

1/1 point (ungraded)  
A sum-of-products expression involving 3 variables with greater than 2 product terms can *always* be simplified to a sum-of-products expression using fewer product terms.

☐ True


☒ False



Submit

Minimal Sum Of Products

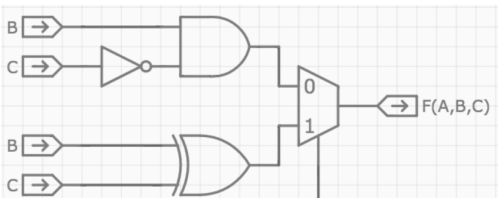10/10 points (ungraded)  
A 6.004 intern at Intel has designed the combinational circuit shown below. His boss can't figure out what it does and has asked for your help.



Calculator



A) Your first task is to fill out  $F(A,B,C)$  in the truth table below:

$A$	$B$	$C$	$F(A,B,C)$
0	0	0	<div>0</div> ✓
0	0	1	<div>0</div> ✓
0	1	0	<div>1</div> ✓
0	1	1	<div>0</div> ✓
1	0	0	<div>0</div> ✓
1	0	1	<div>1</div> ✓
1	1	0	<div>1</div> ✓
1	1	1	<div>0</div> ✓

B) Now, express  $F(A,B,C)$  in minimal sum-of-products form. Hint: use a Karnaugh map!

anot(b)c + bnot(c)

 ✓

C) The boss isn't quite sure what it means but he knows his engineers are always impressed if he asks "is the circuit universal?" Is it? Choose YES or NO.

☒ YES


☐ NO



Submit
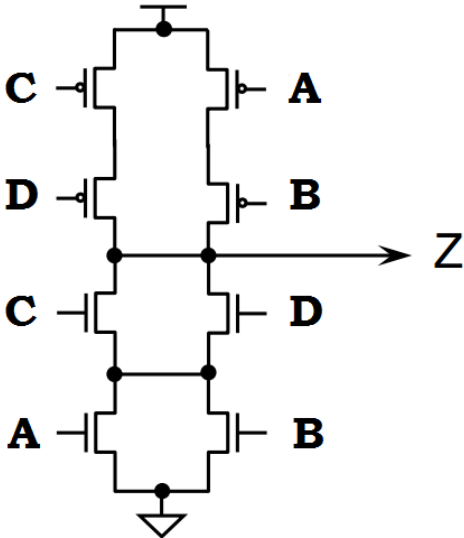
### Minimal Sum Of Products

1/1 point (ungraded)  
Hapless Logic, Inc has found a bunch of CMOS curcuits one of which is shown below:



Hapless Logic has forgotten what function,  $H(A,B,C,D)$ , this circuit computes so they need your help. Give a Boolean sum-of-products expression for  $H(A,B,C,D)$  consistent with the pulldown shown above.

not(c)not(d) + not(a)not(b) ✓

Submit

### Discussion

Hide Discussion

Topic: 4. Combinational Logic / Tutorial : Minimal Sum Of Products

Add a Post

Show all posts	▼	by recent activity	▼
?	Can't understand q2 $\rightarrow$ c	2	▼
In the lecture i understand that any sum of product i can represent it using NAND NAND & NOR NOR but answer of that question try t...			
✓	Universal gate ?	3	▼
In Question 2 my gate ends up as XOR if A=logical 1 ...is XOR universal gate ?			

< Previous

Next >



## edX

- About
- Affiliates
- edX for Business
- Open edX
- Careers
- News

## Legal

- Terms of Service & Honor Code
- Privacy Policy
- Accessibility Policy
- Trademark Policy
- Sitemap

## Connect

- Blog
- Contact Us

Calculator

[Help Center](#)  
[Media Kit](#)  
[Donate](#)



© 2021 edX Inc. All rights reserved.  
深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)