



< Previous

✓

✓

✓

✓

✓

✓

✓

✓

✓

✓

✓

✓


Next >

### LE3.3

🔖 Bookmark this page
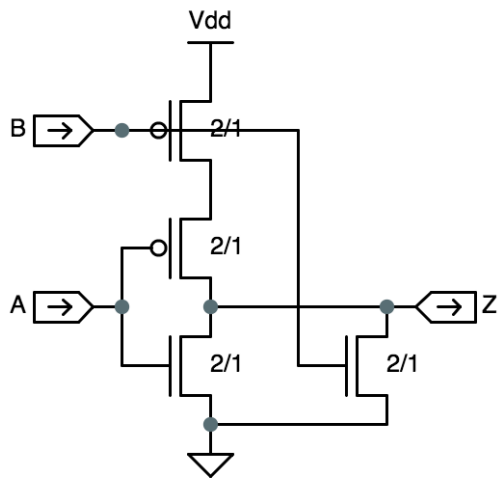
#### LE3.3.1: CMOS Truth Table

4/4 points (ungraded)  
Here's another simple CMOS circuit with series PFETs for the pullup circuit and parallel NFETs for the pulldown circuit.



Please fill in the truth table below, giving the value of the output Z for the four possible combinations of the inputs values A and B.

A	B	Z
0	0	<div>1</div> ✓
0	1	<div>0</div> ✓
1	0	<div>0</div> ✓
1	1	<div>0</div> ✓

Submit

### Discussion

Topic: 3. CMOS / LE3.3

Hide Discussion

Add a Post

Show all posts ▾

by recent activity ▾

STAFF line over the CMOS?

5

On the **top-left CMOS**, would not it be better ( for clarity ) to have the **line** from input B to the bottom-right CMOS go around t...

< Previous

Next >

Calculator



# edX

- [About](#)
- [Affiliates](#)
- [edX for Business](#)
- [Open edX](#)
- [Careers](#)
- [News](#)

# Legal

- [Terms of Service & Honor Code](#)
- [Privacy Policy](#)
- [Accessibility Policy](#)
- [Trademark Policy](#)
- [Sitemap](#)

# Connect

- [Blog](#)
- [Contact Us](#)
- [Help Center](#)
- [Media Kit](#)
- [Donate](#)



© 2021 edX Inc. All rights reserved.  
深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)