



[← Previous](#)

Next 

LE4.6

 [Bookmark this page](#)




 Calculator

LE4.6.1: Mux Logic

8/8 points (ungraded)

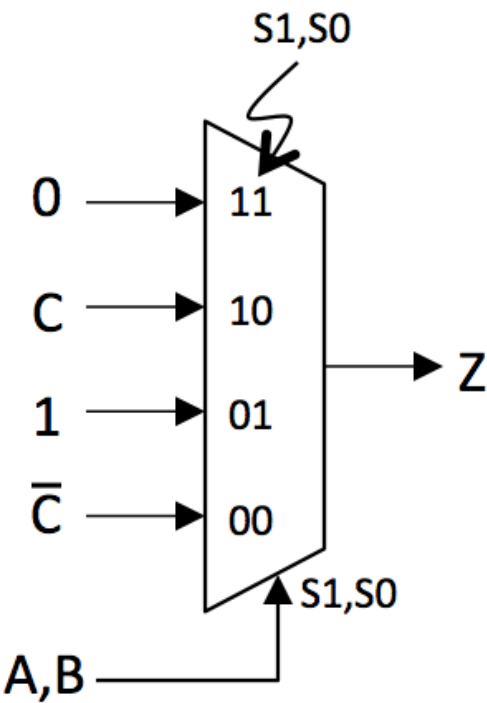Consider the following schematic for a mux-based implementation for a 3-input, 1-output Boolean function.



Please fill in the truth table below, giving the value of the output Z for the eight possible combinations of the inputs values A, B, and C.

A	B	C	Z
0	0	0	<div>1</div> <div>✓</div>
0	0	1	<div>0</div> <div>✓</div>
0	1	0	<div>1</div> <div>✓</div>
0	1	1	<div>1</div> <div>✓</div>
1	0	0	<div>0</div> <div>✓</div>
1	0	1	<div>1</div> <div>✓</div>
1	1	0	<div>0</div> <div>✓</div>
1	1	1	<div>0</div> <div>✓</div>

Submit

Discussion

Hide Discussion

Topic: 4. Combinational Logic / LE4.6

Add a Post

Show all posts

by recent activity

🗨

Can't understand the diagram or how to solve

So a Mux is a data selector given the selector inputs. The selector inputs correspond to the 4 inputs, 0, 1, C and not C. And I'm assu...

3

✓

Can't understand diagram.

I can't understand the information conveyed by the diagram. What is the meaning of the curved arrow? I have no idea about anything...

2

🧮

Calculator

< Previous

Next >

© All Rights Reserved



edX

- [About](#)
- [Affiliates](#)
- [edX for Business](#)
- [Open edX](#)
- [Careers](#)
- [News](#)

Legal

- [Terms of Service & Honor Code](#)
- [Privacy Policy](#)
- [Accessibility Policy](#)
- [Trademark Policy](#)
- [Sitemap](#)

Connect

- [Blog](#)
- [Contact Us](#)
- [Help Center](#)
- [Media Kit](#)
- [Donate](#)



© 2021 edX Inc. All rights reserved.
深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)