

<u>Help</u>

selfpoised >

Next >

<u>Course Progress Dates Course Notes Discussion</u>







< Previous

⊞ Calculator

Leniency

1/1 point (ungraded)

Topic: 3. CMOS / Tutorial: Leniency

In lecture we saw that a 2-input NOR gate might obey the static discipline (i.e., be a valid combinational device) without being a lenient combinational device. Is it possible for an inverter to be a valid combinational device without being lenient?

Yes	
No	
Can't Tell	
•	
Submit	
Leniency	
1/1 point (ungraded) A 2-input AND gate is made from a lenient CMOS 2-input NAND gate followed by a lenient CM AND gate necessarily lenient?	OS inverter. Is the
YesNoCan't Tell	
Submit	
Leniency	
1/1 point (ungraded) If an inverter conforms to our definition of a combinational device, is it necessarily lenient?	
YesNo	
Submit	
Discussion	Hide Discussion

Add a Post

Show all posts

Why the inverter is lenient?
Why in the following questions we are considering inverter to be lenient? Usually in lenient devices we ignore one or other inputs repl...

Leniency tutorial - Problem 1
"Is it possible for an inverter to be a valid combinational device without being lenient?" Each inverter is always lenient. The currently...

The Number of Inputs not specified.
In CMOS Tutorial, the last problem "If an inverter conforms to our definition of a combinational device, is it necessarily lenient?" Beca...

Previous

Next >

© All Rights Reserved



edX

About

Affiliates

edX for Business

<u>Open edX</u>

Careers

<u>News</u>

Legal

Terms of Service & Honor Code

Privacy Policy

<u>Accessibility Policy</u>

Trademark Policy

<u>Sitemap</u>

Connect

<u>Blog</u>

Contact Us

Help Center

Media Kit

Donate















© 2021 edX Inc. All rights reserved.

深圳市恒宇博科技有限公司 <u>粤ICP备17044299号-2</u>