



< Previous					Next >
-------------------------------	--	--	--	--	---------------------------


WE4.2

Bookmark this page

Video explanation of solution is provided below the problem.

Gates and Boolean Logic

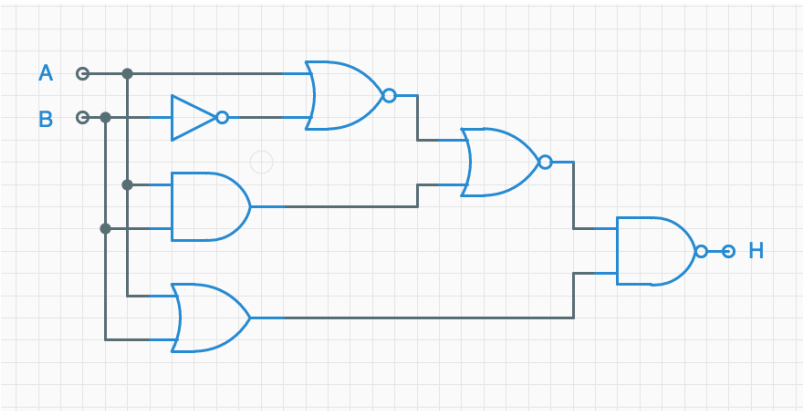4/4 points (ungraded)
Given the circuit shown below, create a truth table that describes the function H that this circuit represents



A	B	H
0	0	<div>1</div> <div>✓</div>
0	1	<div>1</div> <div>✓</div>
1	0	<div>0</div> <div>✓</div>
1	1	<div>1</div> <div>✓</div>

Submit

Gates and Boolean Logic

Sum of Products

A	B	H
0	0	1
0	1	1
1	0	0
1	1	1

(Caption will be displayed when you start playing the video.)

▶ 0:00 / 0:00

▶ 1.0x

🔊

🔍

CC

🗣

Video
[Download video file](#)

Transcripts
[Download SubRip \(.srt\) file](#)
[Download Text \(.txt\) file](#)

🧮 Calculator

Discussion

Hide Discussion

Topic: 4. Combinational Logic / WE4.2

Add a Post

Show all posts

by recent activity

Function H

Another way to find an expression for the function H is by focusing in all the cases that make $H=0$. In this case, $\text{not}(H) = A$ and no...

9

what is a single CMOS gate

Hello, I can follow most of the courses material very well, but I still have a problem in understanding of what is a single CMOS gate. Y...

4

< Previous

Next >

© All Rights Reserved



edX

- About
- Affiliates
- edX for Business
- Open edX
- Careers
- News

Legal

- Terms of Service & Honor Code
- Privacy Policy
- Accessibility Policy
- Trademark Policy
- Sitemap

Connect

- Blog
- Contact Us
- Help Center
- Media Kit
- Donate



Calculator



© 2021 edX Inc. All rights reserved.
深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)