













< Previous



 


 



 



Next >


LE8.2

 Bookmark this page

Next, you turn to the problem of pipelining your adders for maximum throughput. You start by pipelining your 4×4 combinational adder, using ideal (zero-delay) registers inserted at strategic positions:

The diagram below has a single place available for registers on each wire. Indicate how many registers should be added on each wire by dragging the appropriate number of registers to each wire to produce a maximum-throughput pipelined implementation of the 4 by 4 adder.

You may consider printing the image and drawing contours to show the pipeline stage boundaries, and then counting how many pipeline stage boundaries are on each wire to know how many registers to put on each wire. Use the minimum number of registers necessary to maximize throughput. Remember to put registers on all outputs. If a wire does not need any registers, do not drag any registers to that wire.

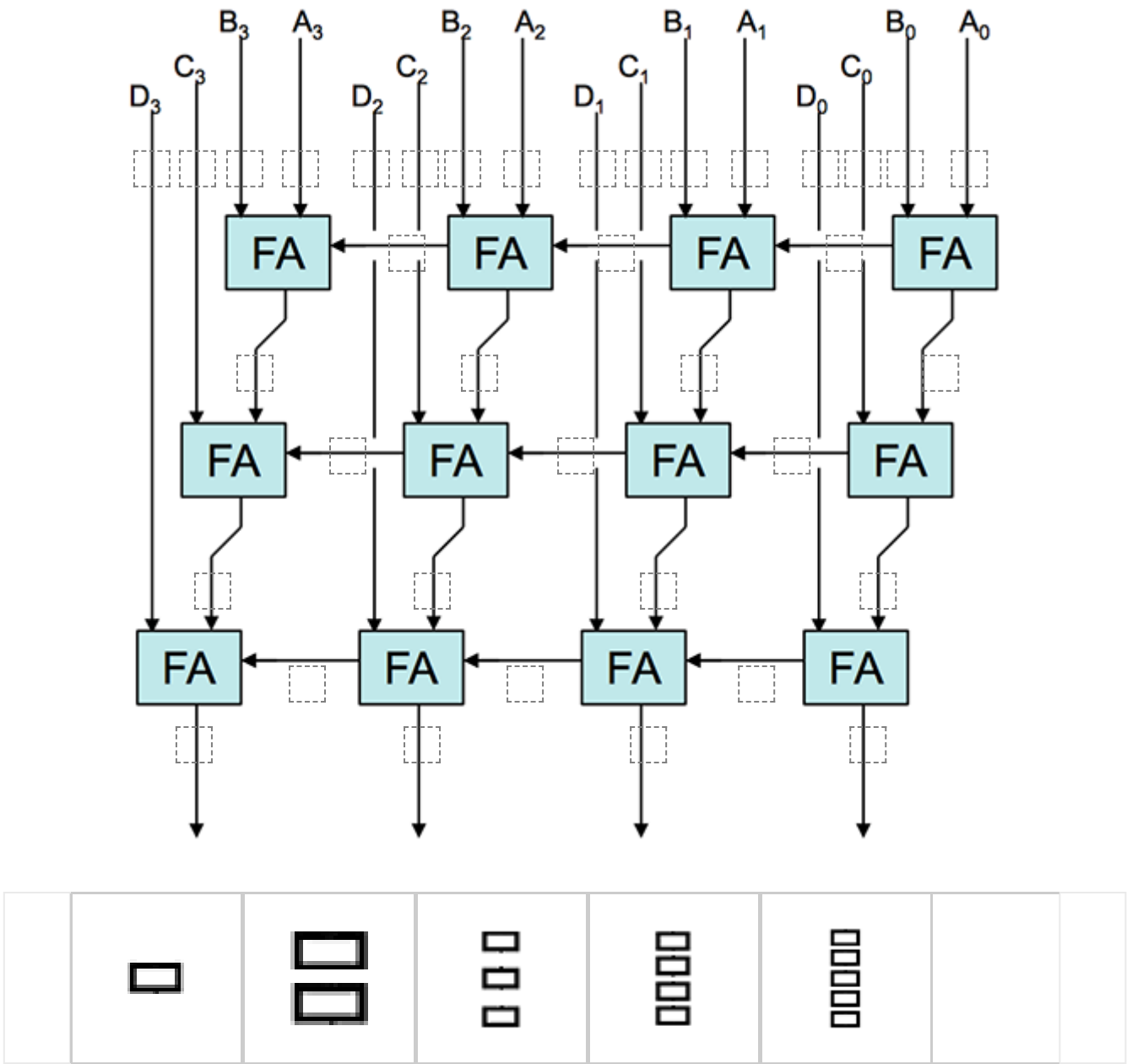

Finally, consider generalizing the pipelined adder to add N k-bit numbers.

Using $\Theta(\dots)$ notation, give asymptotic latency, throughput, and hardware cost of a pipelined adder capable of adding N k-bit quantities. Give expressions in terms of N and k.

Latency $\Theta(\dots)$:

Throughput $\Theta(\dots)$:


Hardware Cost $\Theta(\dots)$:

Submit

Discussion

Topic: 8. Design Tradeoffs / LE8.2

Add a Post

Show all posts	by recent activity
 Grader too strict	1
<input checked="" type="checkbox"/> Hardware cost of generalized adder The explanation says "For every adder in the circuit, we need to add registers for every stage in the pipeline, making sure that each i...	5
<input checked="" type="checkbox"/> [Staff] How registers get counted in \Theta notation? Hello, Please give us clear explanation of how registers get counted in \Theta notation for the last question about Hardware Cost	2
<input checked="" type="checkbox"/> Alternative pipeline	2

< Previous

Next >

© All Rights Reserved



edX

- About
- Affiliates
- edX for Business
- Open edX
- Careers
- News

Legal

- Terms of Service & Honor Code
- Privacy Policy
- Accessibility Policy
- Trademark Policy
- Sitemap

Connect

- Blog
- Contact Us
- Help Center
- Media Kit
- Donate



 Calculator

© 2021 edX Inc. All rights reserved.

深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)