<u>Course</u>

**Discussion** 

<u>Help</u>

selfpoised ~

<u>Progress</u>

★ Course / 13. Building the Beta / Worked Examples

<u>Dates</u>

**(** 

✓ Previous
WE13.2
□ Bookmark this page

**■** Calculator

Video explanation of solution is provided below the problem.

For all Beta related questions, you should make use of the <u>Beta documentation</u>, the <u>Beta Instruction Summary</u>, and the <u>Beta Diagram</u>.

#### **Beta Control Signals**

11/11 points (ungraded)

Following is an incomplete table listing control signals for several instructions on an unpipelined Beta. You may wish to consult Beta diagram and instruction set summary handouts.

The operations listed include two existing instructions and three proposed additions to the Beta instruction set:

```
LDX(Ra, Rb, Rc) // Load, double indexed

EA ← Reg[Ra] + Reg[Rb]

Reg[Rc] ← Mem[EA]

PC ← PC + 4

MVZC(Ra, literal, Rc) // Move constant if zero

If Reg[Ra] == 0 then Reg[Rc] ← SXT(literal)

PC ← PC + 4


STR(Rc, C) // Store relative

EA ← PC+4+4*SEXT(C)

Mem[EA] ← Reg[Rc]


PC ← PC + 4
```

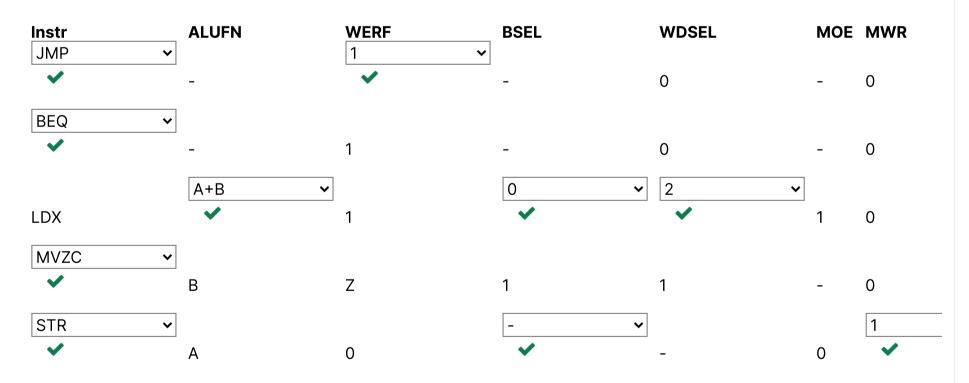
In the following table, - represents a "don't care" or unspecified value; Z is the value (0 or 1) output by the 32-input NOR in the unpipelined Beta diagram. Your job is to complete the table by filling in all the missing values.



Submit

#### **Beta Control Signals**

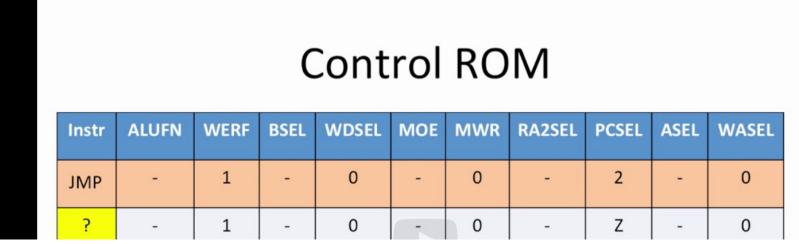

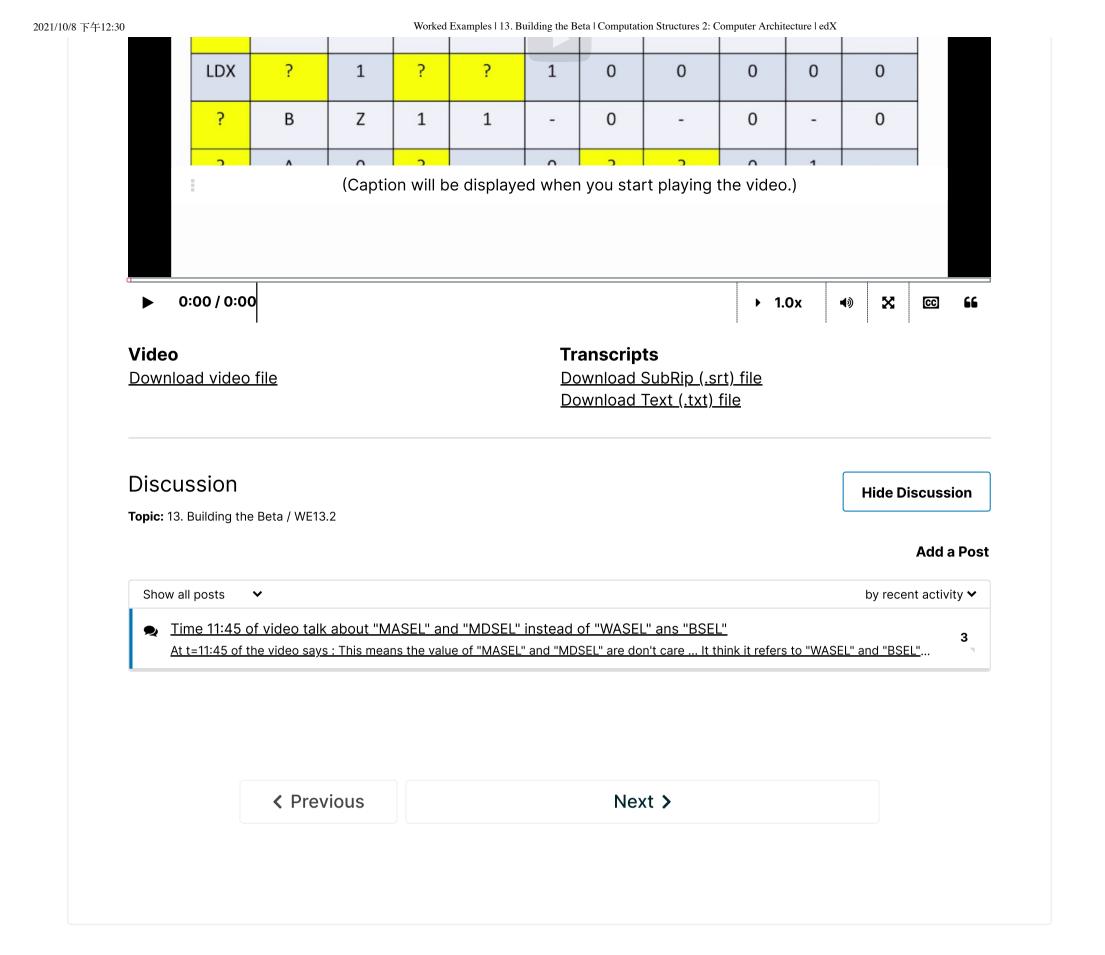

© All Rights Reserved



### edX

**About** 

**Affiliates** 

edX for Business

<u>Open edX</u>

**Careers** 

<u>News</u>

# Legal

Terms of Service & Honor Code

**Privacy Policy** 

**Accessibility Policy** 

<u>Trademark Policy</u>

<u>Sitemap</u>



## **Connect**

<u>Blog</u>

**Contact Us** 

Help Center

Media Kit

**Donate** 















© 2021 edX Inc. All rights reserved.

深圳市恒宇博科技有限公司 <u>粤ICP备17044299号-2</u>