

[Course](#)

[Progress](#)

[Dates](#)

[Course Notes](#)

[Discussion](#)

[🏠 Course](#) / [6. Finite State Machines](#) / [Lecture Videos \(42:27\)](#)



< Previous

 ✓ 

 ✓

 ✓

 ✓

 ✓

 ✓

 ✓

 ✓

 ✓

 ✓


Next >

# LE6.4

 Bookmark this page

## LE6.4.1 Metastability in latches

6/6 points (ungraded)

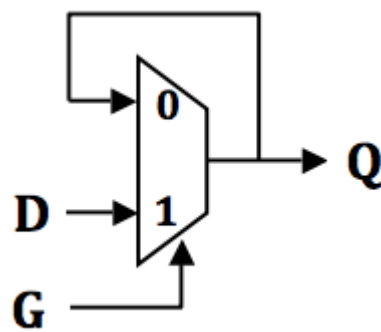

Assume that we have made a transparent latch using a lenient 2-input MUX as shown above. The lenient MUX has a propagation delay of  $t_{PD}$  and a contamination delay of  $t_{CD}$ .

A certain sequence of inputs -- violating the dynamic discipline -- has caused the Q output to assume an invalid voltage. You have observed the voltage at Q at this value for an interval many times larger than  $t_{PD}$ , despite valid stable inputs at D and G during this interval.

For each of the following statements, please indicate either TRUE or FALSE, assuming you are observing an invalid Q output after this relatively long interval of valid D and G inputs.

(A) The G input must be 0.

☒ True

☐ False



(B) The D input must be 1.

☐ True

☒ False



(C) Setting and holding G=1 (while D remains valid and stable) will assure a stable value at Q after a delay of  $t_{PD}$ .

☒ True

☐ False



(D) Setting and holding G=1 for  $t_{PD}$  and returning it to 0 for another  $t_{PD}$  (while D remains valid and stable) will assure that the value at D appears at Q.

☐ True

☒ False



(E) If the inputs remain unchanged (stable and valid) for an interval of T seconds, the probability of a valid Q output at the end of this interval increases exponentially with T.

☒ True

☐ False



(F) Assuming the valid stable inputs remain at D and G, once Q leaves the metastable state and reaches a valid logic level it is guaranteed to have the same value as D.

☐ True

☒ False



Submit

Discussion

Hide Discussion

Topic: 6. Finite State Machines / LE6.4

Add a Post

Show all posts	▼	by recent activity	▼
💬	Increasing exponentially.	3	▼
✓	Why D false? Hello, Can you explain why we need G=1 for 2*t_pd and not single t_PD to guarantee propagation of D to Q? **" If G had been 1 for 2...	3	▼

< Previous

Next >



edX

- About
- Affiliates
- edX for Business
- Open edX
- Careers
- News

Legal

- Terms of Service & Honor Code
- Privacy Policy
- Accessibility Policy
- Trademark Policy
- Sitemap

Calculator

# Connect

[Blog](#)

[Contact Us](#)

[Help Center](#)

[Media Kit](#)

[Donate](#)



© 2021 edX Inc. All rights reserved.  
深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)